
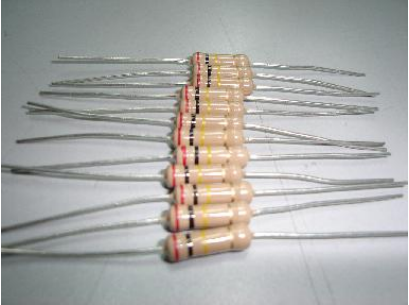

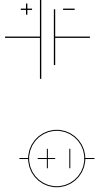

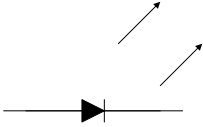
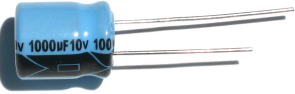
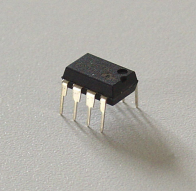
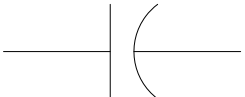
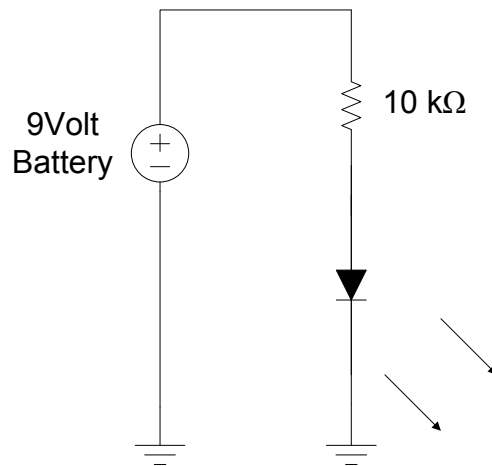


# Circuit Elements

<b>Battery</b>		<b>Resistor</b>	<b>Light Emitting Diode (LED)</b>	
				
red wire +	black wire -		long lead anode +	short lead cathode -
				
<b>Capacitor</b>		<b>555 Timer</b>		
				
long lead no stripe +	short lead stripe -	<input type="checkbox"/> GND <input type="checkbox"/> VCC <input type="checkbox"/> TRIG <input type="checkbox"/> DIS <input type="checkbox"/> OUT <input type="checkbox"/> THRSH <input type="checkbox"/> RESET <input type="checkbox"/> CTRL		
				

## Light Emitting Diode (LED) Circuit



## 555 Timer Circuit

